

# First Exercise

Fundamentals Of Electronics - a.a. 2018-2019 - University of Padua (Italy)

Pietro Prandini (mat. 1097752)

April 24, 2019

## 1 Audio amplifier

### 1.1 Voltage gain and frequency domain

#### 1.1.1 Netlist

```
* Audio Amplifier – Voltage gain and frequency domain (ideal op. amp.)
*****
* 1st Exercise – Fundamentals Of Electronics – a.a. 2018–2019 – UniPD – 1 of 4 *
*                               Pietro Prandini – mat. 1097752                               *
*                                                                                               *
* This work is licensed under the Creative Commons Attribution–ShareAlike 4.0 *
* International License. To view a copy of this license , visit                               *
* http://creativecommons.org/licenses/by-sa/4.0/ or send a letter to Creative *
* Commons, PO Box 1866, Mountain View, CA 94042, USA. *
*****

* Ideal Operational Amplifier subcircuit
.LIB opamp.sub

* Amplifiers
XU1 V- V+ Vo opamp Aol=100k GBW=10meg

* Capacitances
C2 V+ Vi 100n

* Generators
Vin Vi 0 100mV DC 0 AC 1 sin(0 100mV 10kHz 0 0 0)

* Resistances
R2 V+ 0 100k
R3 V- 0 1k
R4 Vo V- 10k

* Analysis
.AC DEC 10 1 100k
.backanno

.END
```