

First SPICE Exercise

Fundamentals Of Electronics - a.a. 2018-2019 - University of Padua (Italy)

Pietro Prandini (mat. 1097752)

May 1, 2019

This work is licensed under the Creative Commons Attribution-ShareAlike 4.0 International License. To view a copy of this license, visit <http://creativecommons.org/licenses/by-sa/4.0/> or send a letter to Creative Commons, PO Box 1866, Mountain View, CA 94042, USA.

1 Audio amplifier

1.1 Voltage gain and frequency domain - Ideal op. amp.

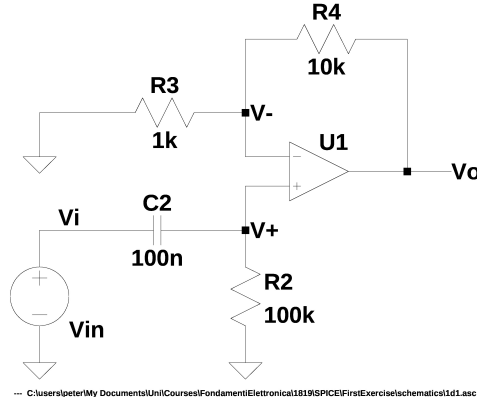


Figure 1: Audio amplifier - Ideal op. amp.

By the analysis of the figure 1's circuit, It's possible to calculate the node V_+ voltage from the ratio of the voltage divider formed by R_2 and C_2 , infact the node V_+ voltage is the same voltage of the resistance R_2 (equation 1).

$$V_+(s) = V_{in}(s) \frac{R_2}{R_2 + \frac{1}{sC_2}} = V_{in}(s) \frac{R_2}{R_2 + \frac{1}{sC_2}} \frac{sC_2}{sC_2} = V_{in}(s) \frac{sC_2 R_2}{1 + sC_2 R_2} \quad (1)$$

The negative feedback produces the virtual short circuit effect, so the V_- and the V_+ voltages have virtually the same value (equation 2), and, because of the fact that the ideal operational amplifier U_1 isn't absorbe current from the V_- and the V_+ nodes, the current of I_{R_4} is the same current of I_{R_3} (equation 3). The current I_{R_3} is calculated by the Ohm law (equation 4).

$$V_- = V_+ \quad (2)$$

$$I_{R_4} = I_{R_3} \quad (3)$$

$$I_{R_3} = \frac{V_-}{R_3} = \frac{V_+}{R_3} \quad (4)$$

By combining the past considerations it's possible to define the output voltage V_o relating to the voltage input V_{in} (equation 5).

$$V_o(s) = V_+(s) + R_4 I_{R_4} = V_+(s) + R_4 I_{R_3} = V_+(s) + R_4 \cdot \frac{V_+(s)}{R_3} = V_+(s) \cdot \left(1 + \frac{R_4}{R_3}\right) = V_{in}(s) \frac{sC_2 R_2}{1 + sC_2 R_2} \cdot \left(1 + \frac{R_4}{R_3}\right) \quad (5)$$

Consequently of the equation 5, the transfer funtion $V_o(s)/V_{in}(s)$ is described by the equation 6.

$$\frac{V_o(s)}{V_{in}(s)} = \frac{sC_2R_2}{1 + sC_2R_2} \left(1 + \frac{R_4}{R_3}\right) \quad (6)$$

Defining K as in the equation 7 and ω_1 as in the equation 8, the transfer function $V_o(s)/V_{in}(s)$ became in the Bode form (equation 9).

$$K = C_2R_2 \cdot \left(1 + \frac{R_4}{R_3}\right) \quad (7)$$

$$\omega_1 = \frac{1}{C_2R_2} \quad (8)$$

$$\frac{V_o(s)}{V_{in}(s)} = K \frac{s}{1 + s\frac{1}{\omega_1}} \quad (9)$$

Finally it's possible to calculate the frequency domain by the analysis of the transfer function's Bode form (equations 10 and 11).

$$K|_{dB} = 20 \log_{10} |K| = \log_{10} \left| C_2R_2 \cdot \left(1 + \frac{R_4}{R_3}\right) \right| = -19.1722dB \quad (10)$$

$$\log_{10} |\omega_1| = \log_{10} \left| \frac{1}{C_2R_2} \right| = 2.0000 \quad (11)$$

1.2 Voltage output waveform - LT1028 op. amp.

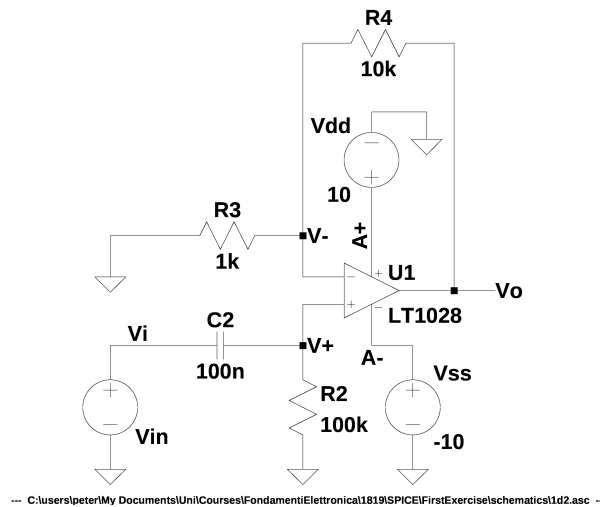


Figure 2: Audio amplifier - LT1028 op. amp.

From now it's considered the circuit of the figure 2.

In order to simulate the waveform output voltage with a sinusoidal voltage input V_{in} with an amplitude of $10mV$ and the frequencies of $1Hz$, $10Hz$ and $10kHz$, it's possible to use a SPICE transient analysis.

1.2.1 Netlist

It's presented the netlist for the SPICE analysis requested.

```
* Audio Amplifier - Waveform
*****
* 1st Exercise - Fundamentals Of Electronics - a.a. 2018-2019 - UniPD - 1 of 4 *
*                               Pietro Prandini - mat. 1097752                               *
*                                                                                               *
* This work is licensed under the Creative Commons Attribution-ShareAlike 4.0 *
* International License. To view a copy of this license, visit                               *
```

```

* http://creativecommons.org/licenses/by-sa/4.0/ or send a letter to Creative *
* Commons, PO Box 1866, Mountain View, CA 94042, USA. *
*****

* Libraries
.LIB LTC.lib

* Amplifiers
XU1 V+ V- A+ A- Vo LT1028

* Capacitances
C2 Vi V+ 100n

* Generators
Vin Vi 0 DC 0 AC 1 sin(0 10mV {F} 0 0 0)
Vdd A+ 0 DC 10
Vss A- 0 DC -10

* Resistances
R2 V+ 0 100k
R3 V- 0 1k
R4 Vo V- 10k

* Analysis
.step param F list 1Hz 10Hz 100Hz
.tran 0 250m 0 1m uic

.END

```

1.2.2 Graph

This graph is the output of the last netlist presented. There are three curves, one for every frequency analyzed (1Hz, 10Hz and 10kHz).

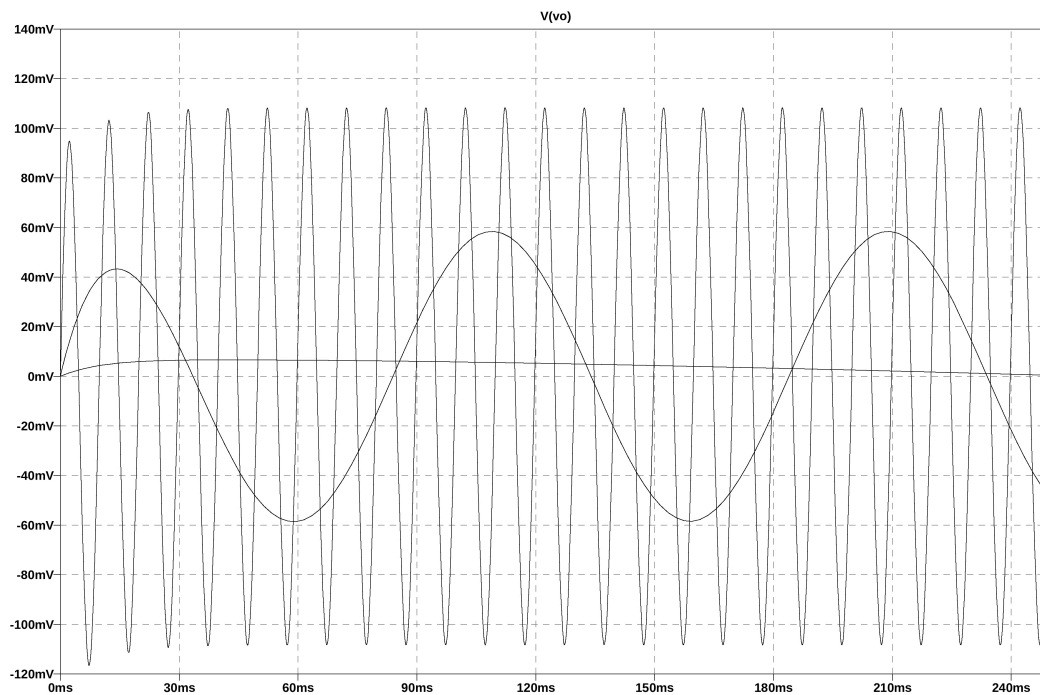


Figure 3: Audio Amplifier - Voltage output waveform

1.3 Bode plot - LT1028 op. amp.

The Bode plot could be generated with a SPICE small signal AC analysis.

1.3.1 Netlist

It's presented the netlist for the SPICE analysis requested.

```
* Audio Amplifier – Bode diagram
*****
* 1st Exercise – Fundamentals Of Electronics – a.a. 2018–2019 – UniPD – 1 of 4 *
*                               Pietro Prandini – mat. 1097752                               *
*                                                                                               *
* This work is licensed under the Creative Commons Attribution–ShareAlike 4.0 *
* International License. To view a copy of this license, visit                               *
* http://creativecommons.org/licenses/by-sa/4.0/ or send a letter to Creative *
* Commons, PO Box 1866, Mountain View, CA 94042, USA. *
*****

* Libraries
.LIB LTC.lib

* Amplifiers
XU1 V+ V– A+ A– Vo LT1028

* Capacitances
C2 Vi V+ 100n

* Generators
Vin Vi 0 DC 0 AC 1 sin(0 10mV {F} 0 0 0)
Vdd A+ 0 DC 10
Vss A– 0 DC –10

* Resistances
R2 V+ 0 100k
R3 V– 0 1k
R4 Vo V– 10k

* Analysis
.step param F list 1Hz 10Hz 100Hz
.ac DEC 10 1 100k

.END
```

1.3.2 Graph

The Bode plot generated could be visible in the figure 4. The continuous line represents the magnitude and the dashed line represents the phase frequency.

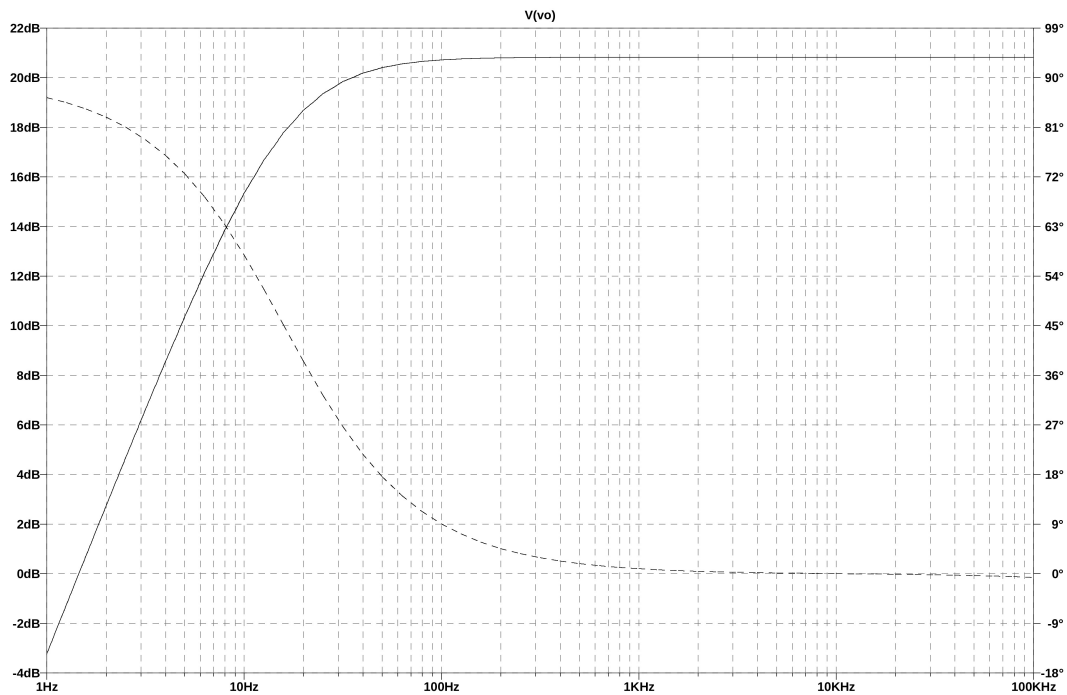


Figure 4: Audio Amplifier - Bode plot

1.4 Saturation - LT1028 op. amp.

The voltage output saturation could be analyzed by giving an abnormally high voltage input to the input. The next netlist analyzes the voltage output with an input with 100V amplitude.

```
* Audio Amplifier - Waveform
*****
* 1st Exercise - Fundamentals Of Electronics - a.a. 2018-2019 - UniPD - 1 of 4 *
*                               Pietro Prandini - mat. 1097752                               *
*                                                                                               *
* This work is licensed under the Creative Commons Attribution-ShareAlike 4.0 *
* International License. To view a copy of this license, visit                               *
* http://creativecommons.org/licenses/by-sa/4.0/ or send a letter to Creative *
* Commons, PO Box 1866, Mountain View, CA 94042, USA. *
*****

* Libraries
.LIB LTC.lib

* Amplifiers
XU1 V+ V- A+ A- Vo LT1028

* Capacitances
C2 Vi V+ 100n

* Generators
Vin Vi 0 DC 0 AC 1 sin(0 100V {F} 0 0 0)
Vdd A+ 0 DC 10
Vss A- 0 DC -10

* Resistances
R2 V+ 0 100k
R3 V- 0 1k
R4 Vo V- 10k
```

```

* Analysis
.step param F list 1Hz 10Hz 100Hz
.tran 0 250m 0 1m uic

.END

```

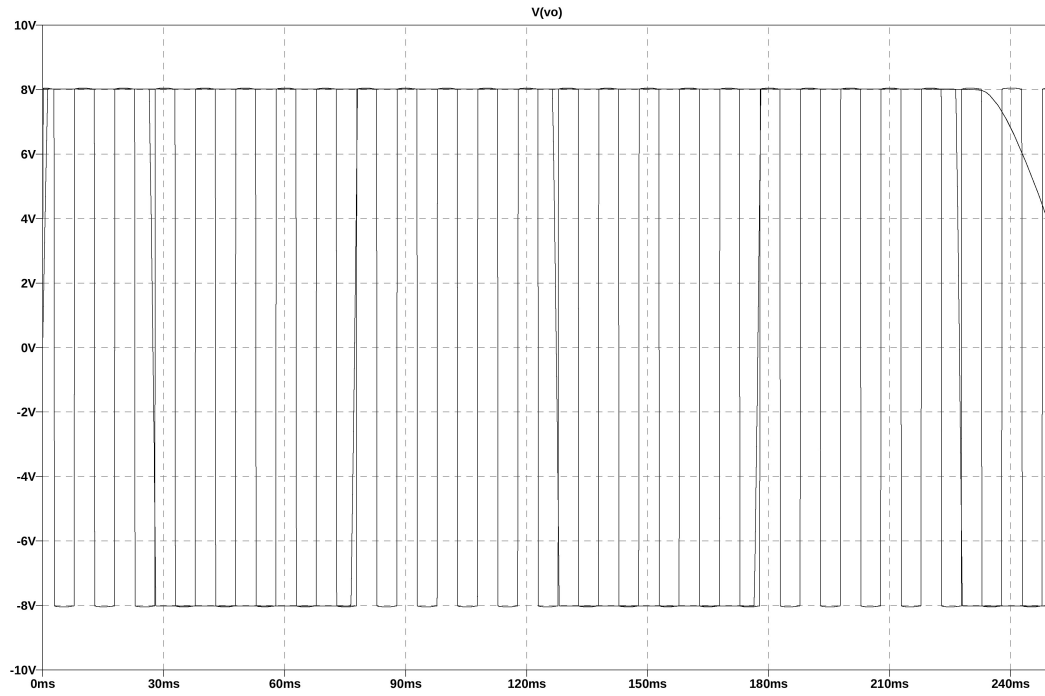


Figure 5: Audio Amplifier - Output voltage saturation

The graph generated (figure 5) makes clear the fact that the voltage output saturation is on $\pm 8V$. So it's possible to calculate which is the highest signal it's accepted by the circuit that avoids the saturation.

$$|V_o(j\omega)| \leq 8V \quad (12)$$

$$\left| V_{in}(j\omega) \frac{j\omega C_2 R_2}{1 + j\omega C_2 R_2} \cdot \left(1 + \frac{R_4}{R_3} \right) \right| \leq 8V \quad (13)$$