

Third SPICE Exercise

Fundamentals Of Electronics - a.a. 2018-2019 - University of Padua (Italy)

Pietro Prandini (mat. 1097752)

June 7, 2019

Contents

1	Differential amplifier with MOS current source	5
1.1	SPICE Operating Point analysis	5

Chapter 1

Differential amplifier with MOS current source

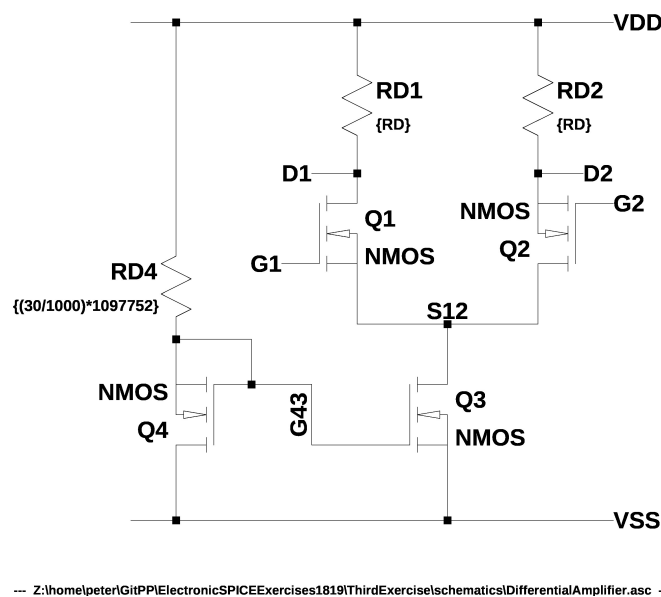


Figure 1.1: Differential amplifier with MOS current source

1.1 SPICE Operating Point analysis

```
* Differential Amplifier
*****
* 3st Exercise – Fundamentals Of Electronics – a.a. 2018–2019 – UniPD – Italy *
*                               Pietro Prandini – mat. 1097752                *
*                                                                           *
* This work is licensed under the Creative Commons Attribution–ShareAlike 4.0 *
* International License. To view a copy of this license, visit              *
* http://creativecommons.org/licenses/by-sa/4.0/ or send a letter to Creative *
* Commons, PO Box 1866, Mountain View, CA 94042, USA.                      *
*****

* Parameters
.param Vt = 0.5V
.param unCox = 200u
.param lambda = 0

.param W12 = 1.25u
```

```

.param L12 = 0.25u

.param W34 = 4.00u
.param L34 = 0.20u

.param RD = 20k

* NMOS model
.model NMOS NMOS VT0 = Vt KP = unCox LAMBDA = lambda

* Resistances
RD1 DDN D1 {RD}
RD2 DDN D2 {RD}
RD4 DDN G43 {(30/1000)*1097752}

* Transistors
MQ1 D1 G1 S12 S12 NMOS W=W12 L=L12
MQ2 S12 G2 D2 D2 NMOS W=W12 L=L12
MQ3 S12 G43 SSN SSN NMOS W=W34 L=L34
MQ4 SSN G43 G43 G43 NMOS W=W34 L=L34

* Voltage sources
VDD DDN 0 +3
VSS SSN 0 -3

* Initial conditions
.ic V(G1) = 0
.ic V(G2) = 0

* Analysis
.op

.END

```

—— Operating Point ——

```

V(ddn):  3          voltage
V(d1):   3          voltage
V(d2):   2.56218     voltage
V(g43):  -2.39538    voltage
V(g1):   0          voltage
V(s12):  2.00589     voltage
V(g2):   0          voltage
V(ssn):  -3         voltage
Id(Mq4): -0.000163831 device_current
Ig(Mq4):  0          device_current
Ib(Mq4):  0.00014194  device_current
Is(Mq4):  2.18912e-005 device_current
Id(Mq3):  2.18913e-005 device_current
Ig(Mq3):  0          device_current
Ib(Mq3): -5.01589e-012 device_current
Is(Mq3): -2.18912e-005 device_current
Id(Mq2): -2.19023e-005 device_current
Ig(Mq2):  0          device_current
Ib(Mq2):  2.19023e-005 device_current
Is(Mq2):  5.56285e-013 device_current
Id(Mq1):  1.99822e-012 device_current
Ig(Mq1):  0          device_current
Ib(Mq1): -1.00411e-012 device_current
Is(Mq1): -9.9411e-013 device_current
I(Rd4):  0.000163831 device_current

```

I(Rd2):	2.18913e-005	device_current
I(Rd1):	1.99822e-012	device_current
I(Vss):	0.000185722	device_current
I(Vdd):	-0.000185722	device_current